

Maria Rice MHR2154
Nolan Tremelling NNT2109
E3083 Electronics Circuits Lab
Experiment 1 Lab Report
Feb 18, 2022

Experiment #1: Measurement of Diode I-V Characteristics Using a Homemade Curve Tracer

In *Figure 1*, *2*, and *3* we can see the I-V curves for a 1N4148 diode, a germanium diode, and a red LED. In finding the I-V curves across a factor for vertical scale voltage to current. For the 1N4148 diode there were $400\mu\text{A}$ per division, resulting from a $400\text{mV}/\text{div}$ channel setting and a $1\text{k}\Omega$ sense resistor. For the germanium diode there was also a $400\mu\text{A}$ per division, resulting from a $400\text{mV}/\text{div}$ channel setting and a $1\text{k}\Omega$ sense resistor. For the red LED there were $280\mu\text{A}$ per division, resulting from a $280\text{mV}/\text{div}$ channel setting and a $1\text{k}\Omega$ sense resistor.

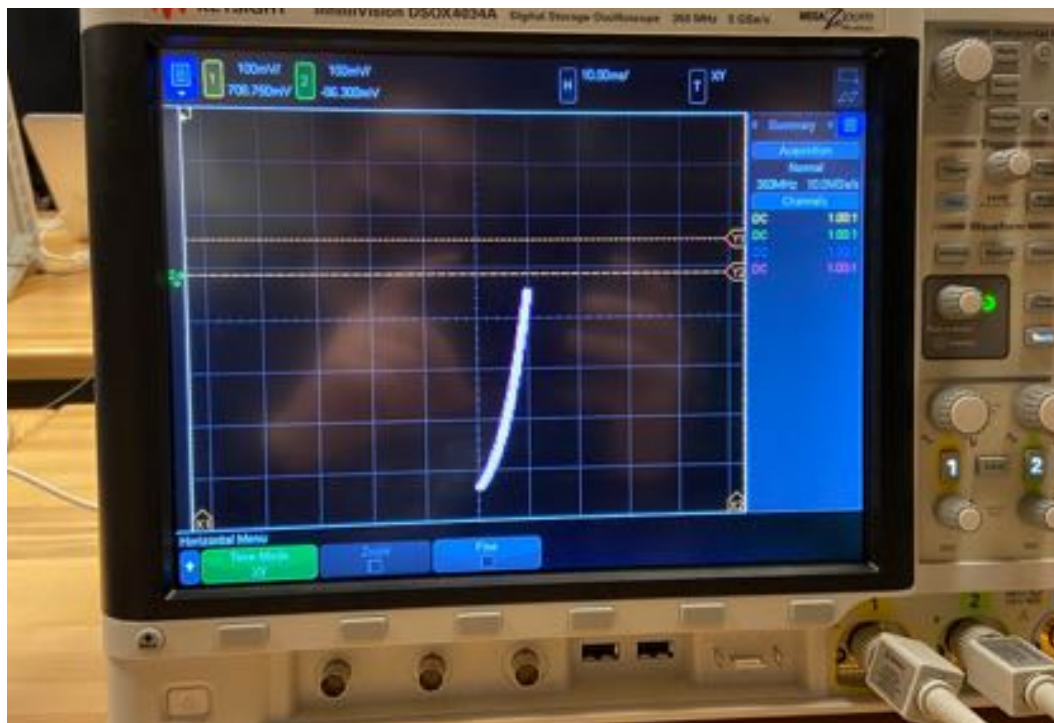


Figure 1: I-V Curve for 1N4148 diode.



Figure 2: I-V Curve for germanium diode.



Figure 3: I-V Curve for red LED.

Experiment #2: Fun with Diodes I: Rectifiers

Half-Wave Rectifier

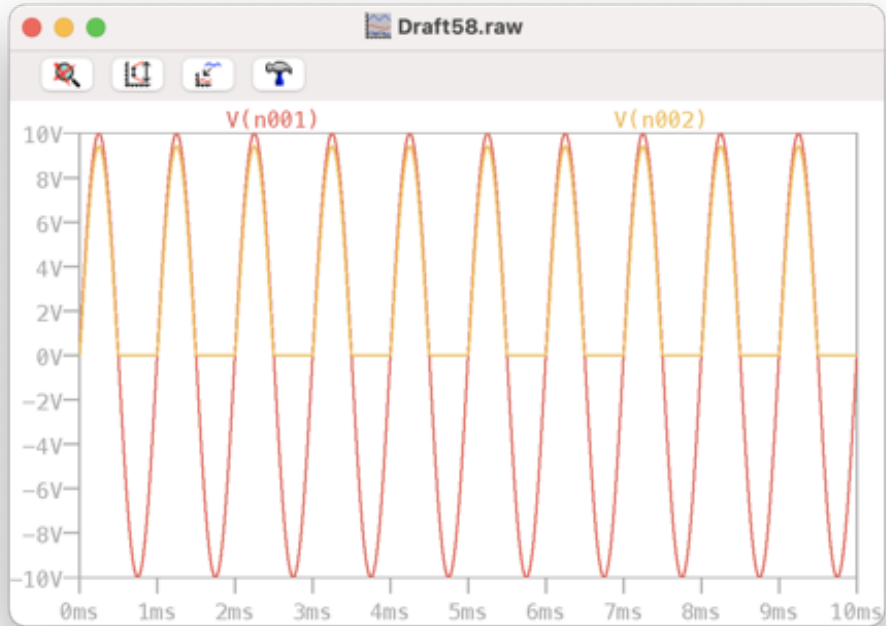


Figure 4: Simulation of half-wave rectifier simulation output.

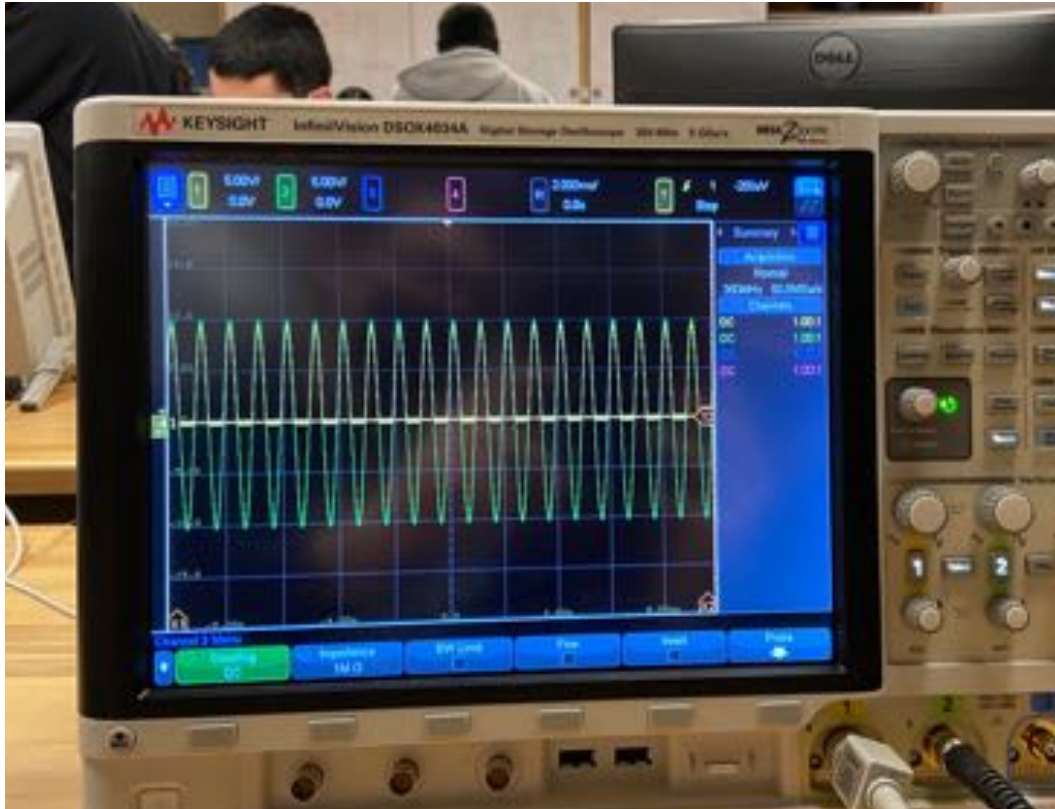


Figure 5: Half-wave rectifier output.

Peak Rectifier

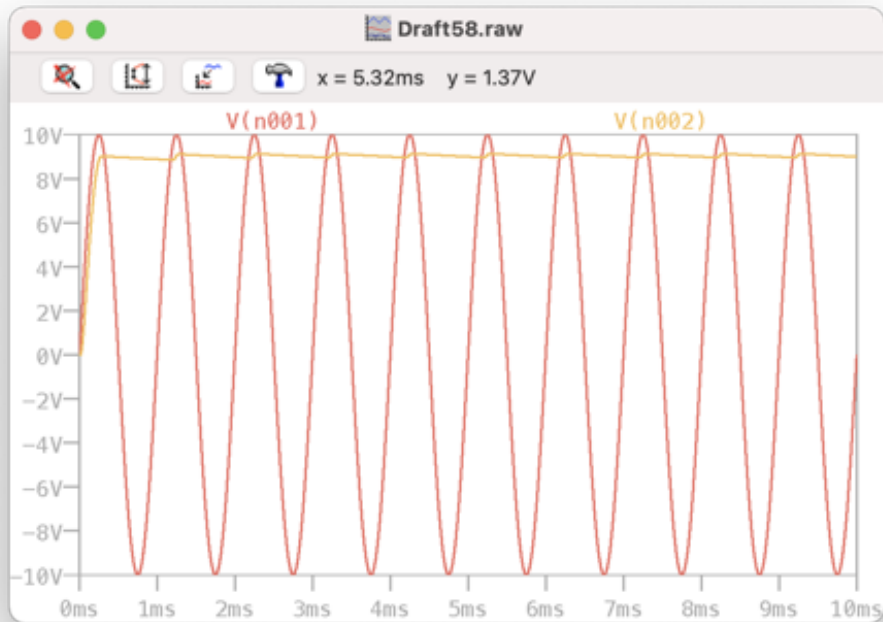


Figure 6: Peak rectifier with RL of $1k\Omega$, C of $47\mu F$ simulation output.

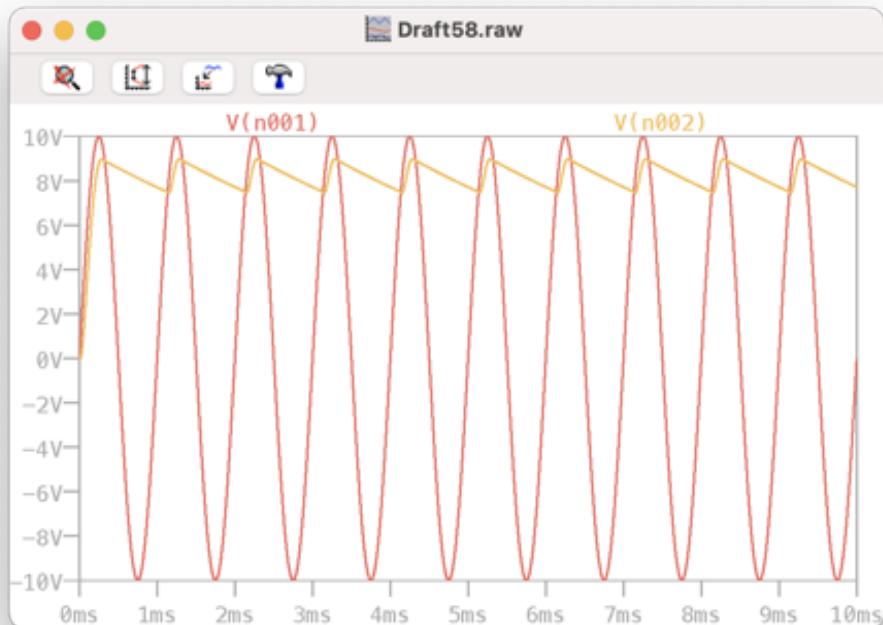


Figure 7: Peak rectifier with RL of 100Ω , C of $47\mu F$ simulation output.

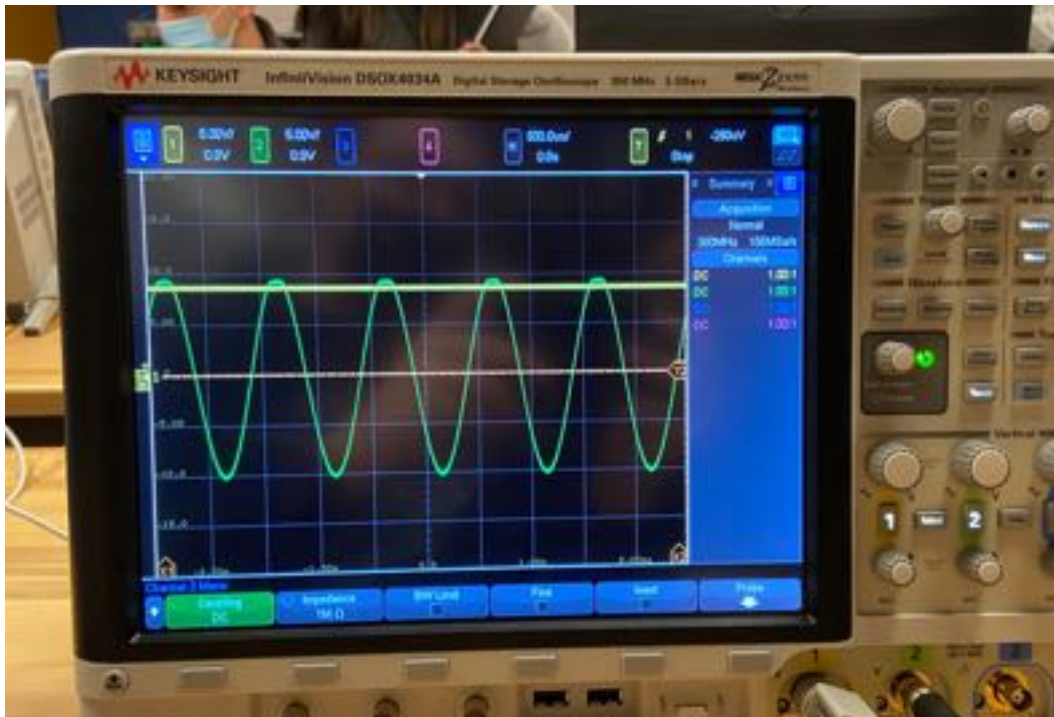


Figure 8: Peak rectifier with RL of $1k\Omega$, C of $47\mu F$ output.

Note: While we measured a peak rectifier with RL of 100Ω , we forgot to take a photo. The waveform generated was much like that of *Figure 8*, differing only in that the voltage across the resistor dropped more than in *Figure 8*.

Precision Rectifier

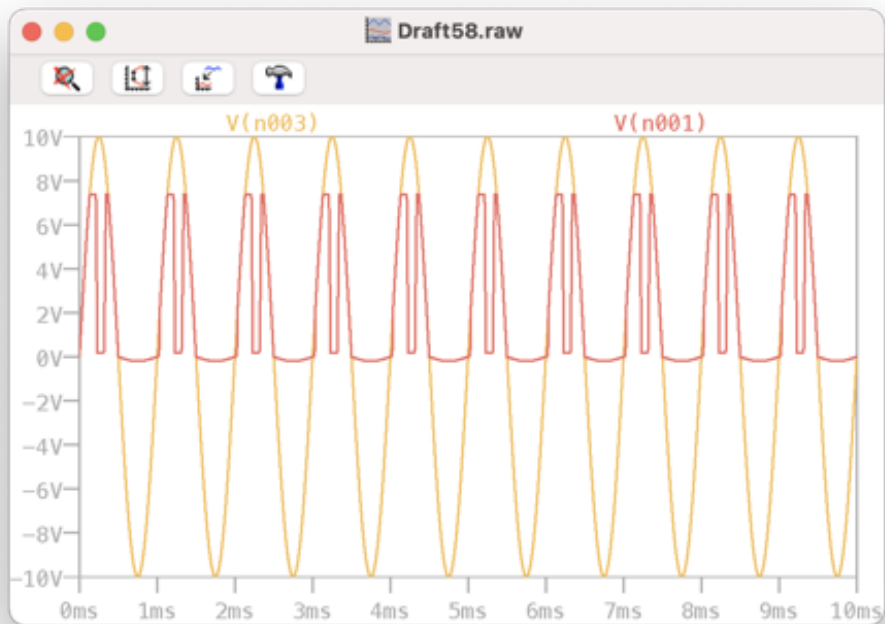


Figure 9: Precision rectifier simulation output.

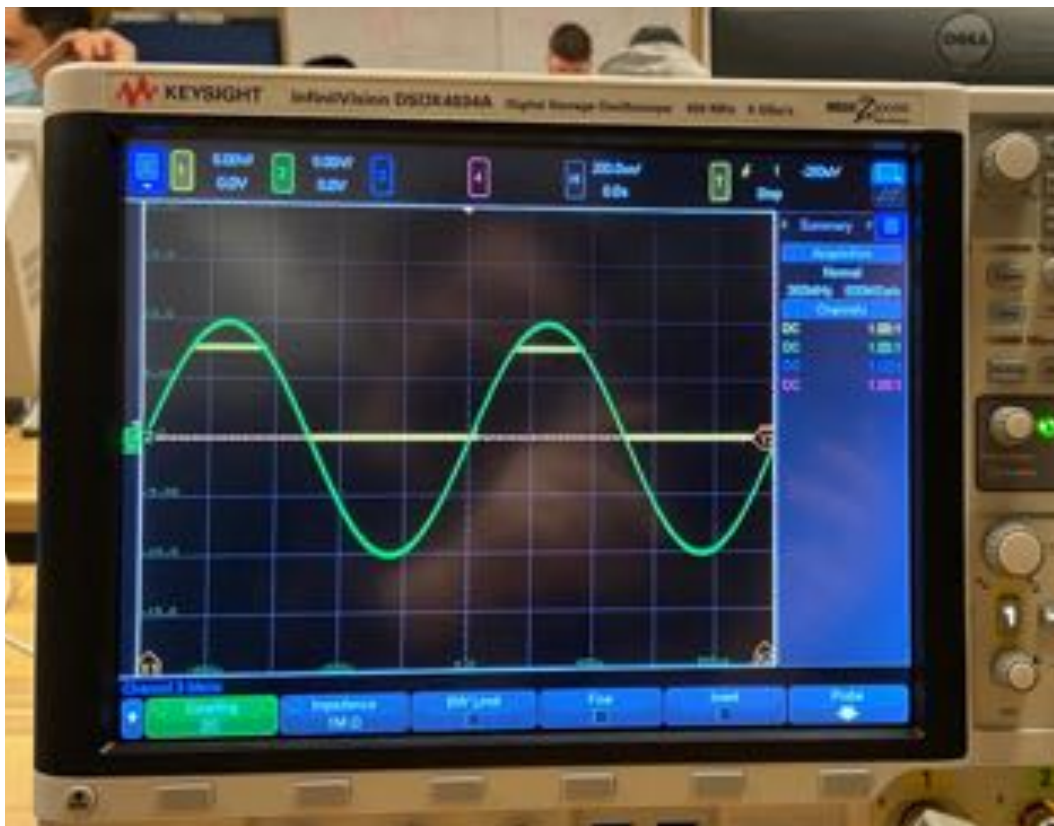


Figure 10: Precision rectifier output.

Experiment #3: Fun with Diodes II: Limiting and Clamping Circuits

Diode Limiter



Figure 11: Diode limiter simulation output.

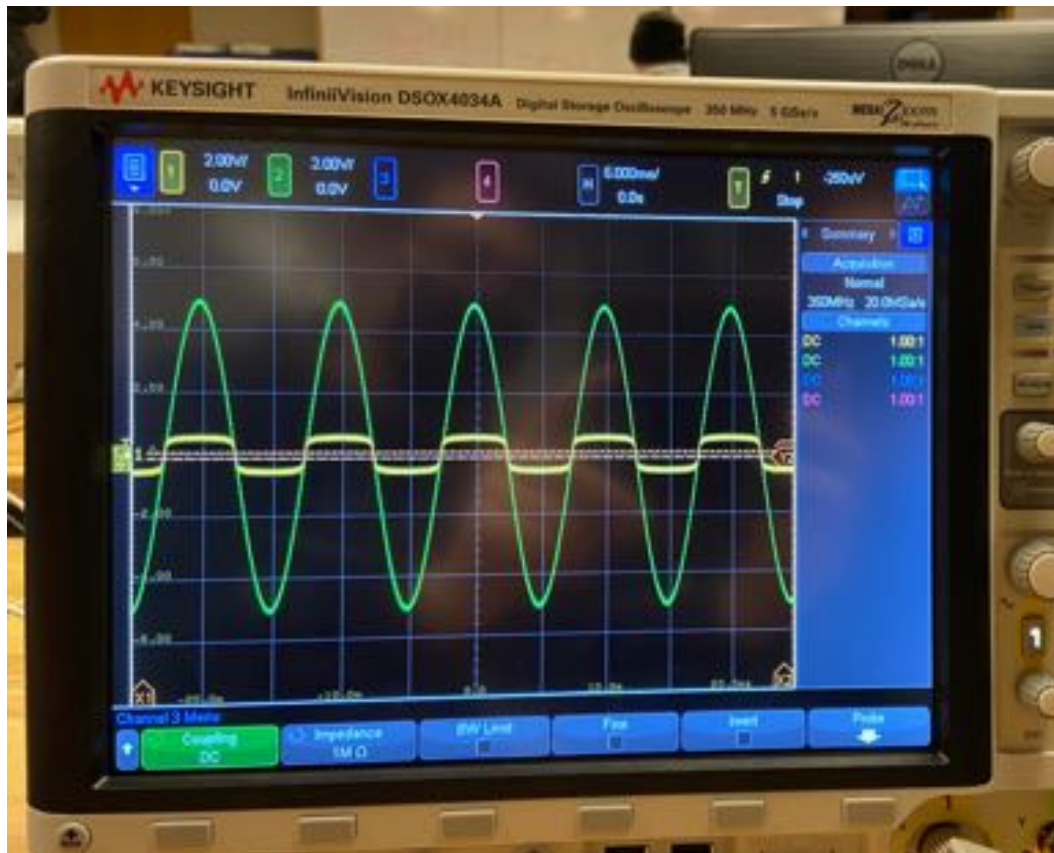


Figure 12: Diode limiter output.

Clamped Capacitor

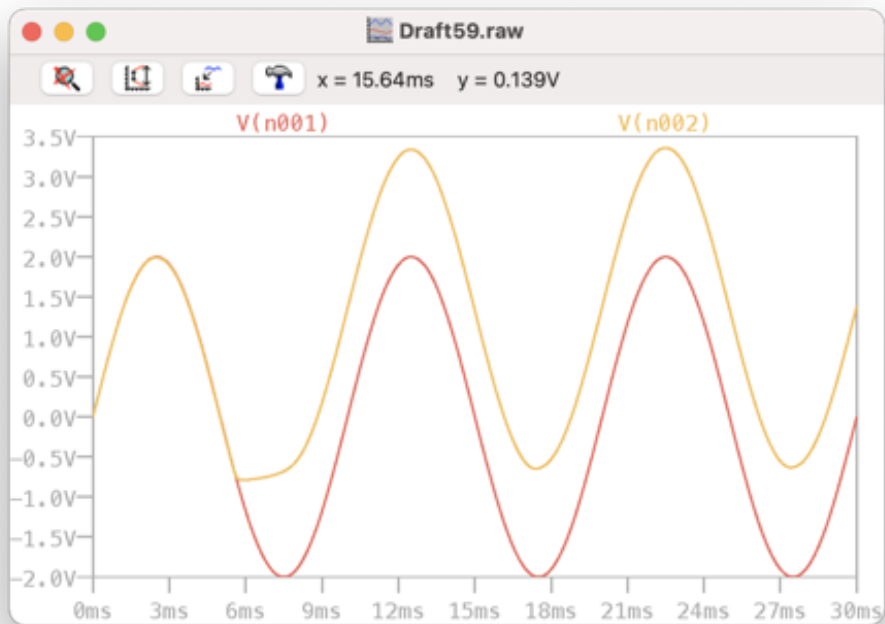


Figure 13: Clamped capacitor simulation output. Note that the peak voltage was approximately 3.5V.

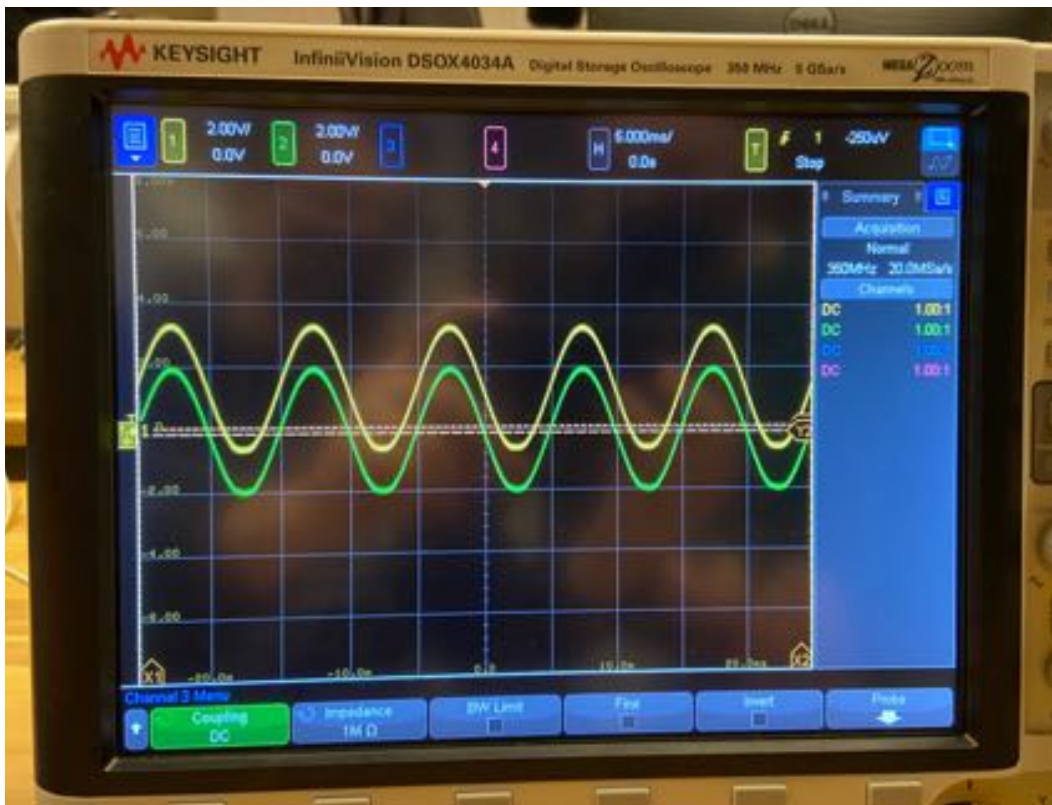


Figure 14: Clamped capacitor output.

Voltage Doubler

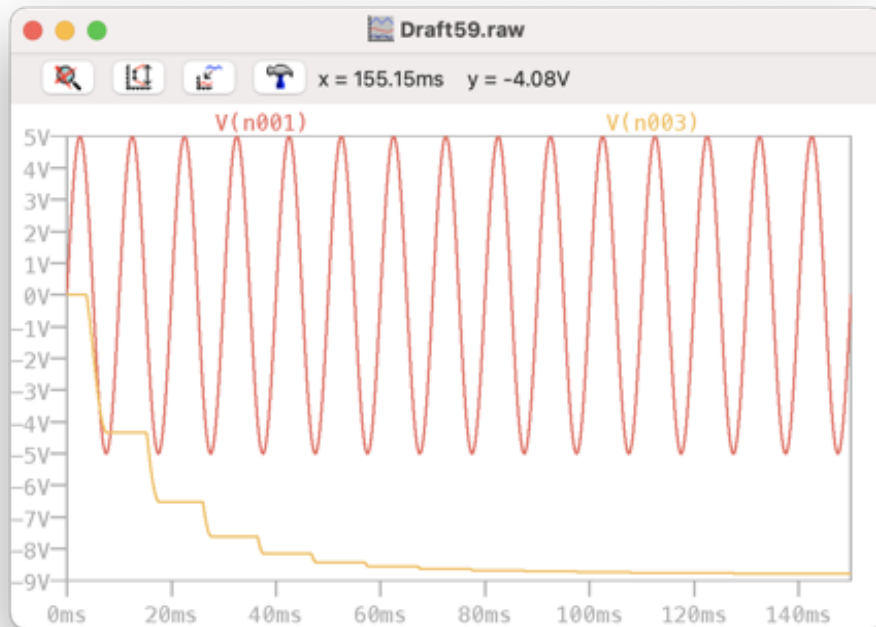


Figure 15: Voltage doubler simulation output.

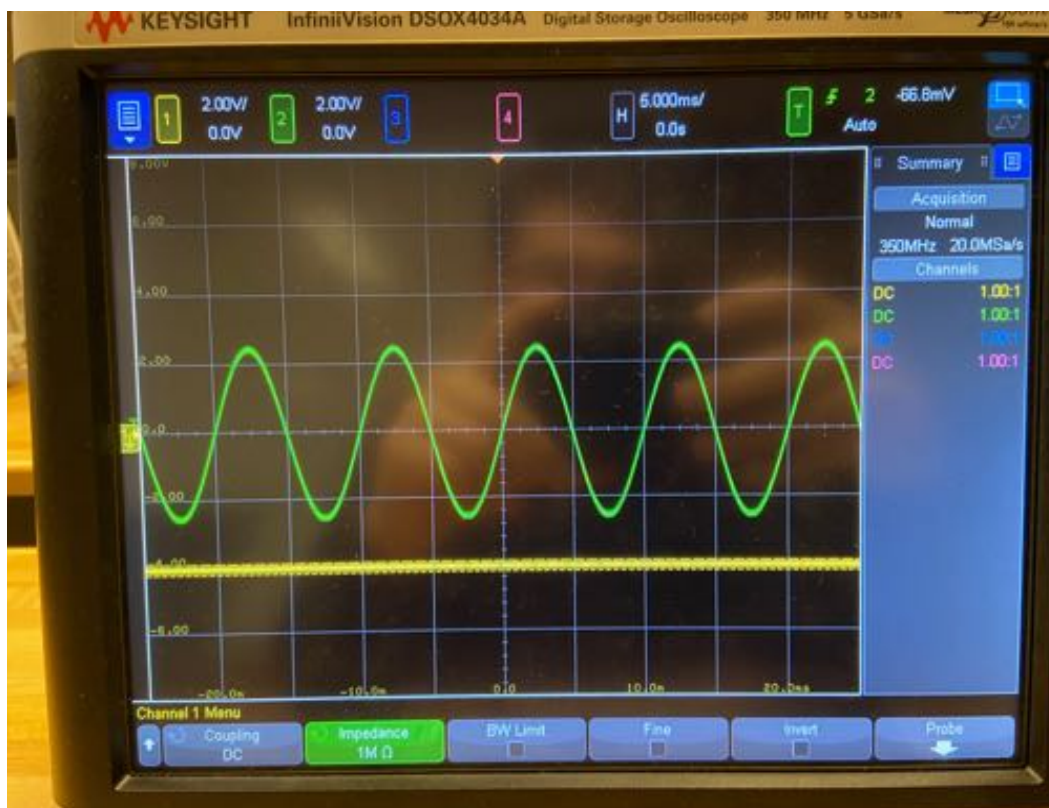


Figure 16: Voltage doubler output. A peak voltage of $\sim 4V$ is observed.

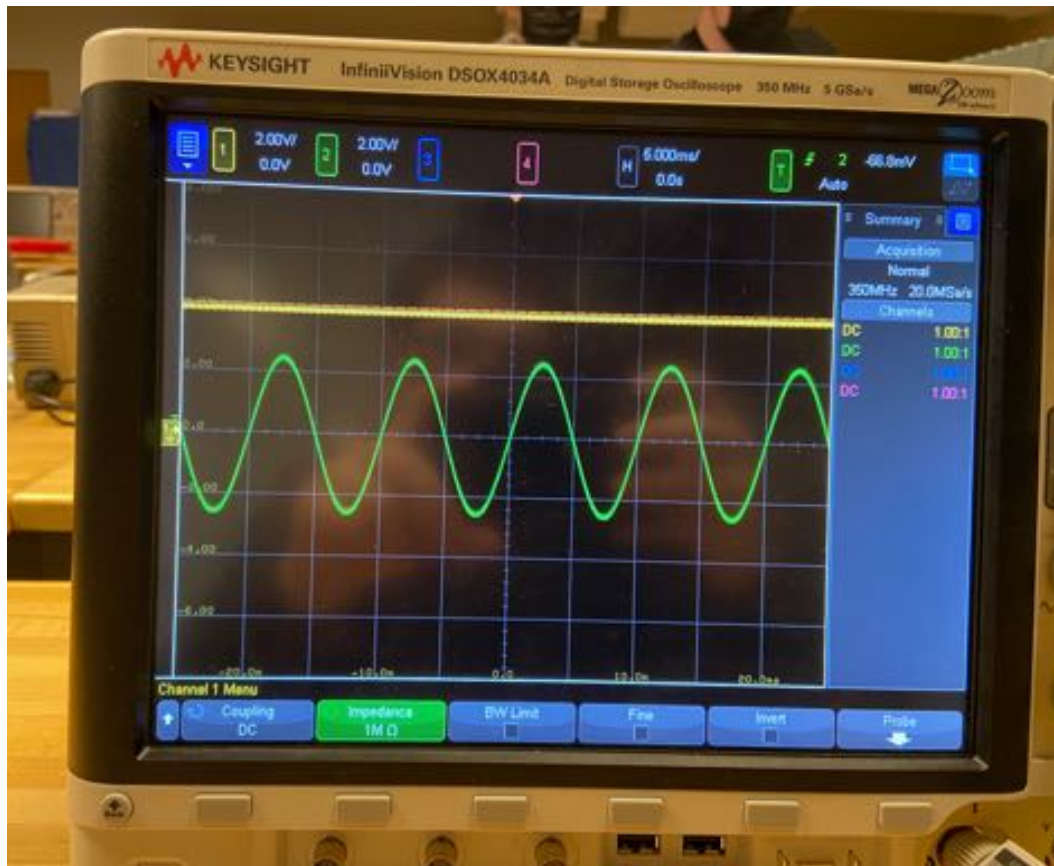


Figure 17: Voltage doubler output with diode reversed. A peak voltage of $\sim 4V$ is observed.